UNIT-1

1)

9 Waite shoot notes on binary number systems!


Ans: Bi Means ?, It is a number system which uses only two different Symbols they are or I. Hence xadix of the number system is ?! Starting from the decimal Point moving toward left are ? ???! and moving toward sight are 2, 22, 53

رط What are the charactesstics of Digital Systems?

Ans: The main characterstic of digital system is that they Process and sepsesent information using discreate values, typically binary Lo's and 1's).

Realize the expression F= A'+13(c'+0') uging 10gic gates! CJ

Given expression F= A+B(C+D') Ans:

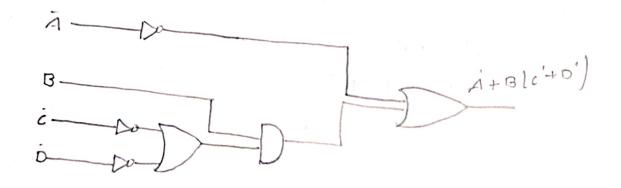


dj Why NANO and NOR gates one called universal gates? Ans: NAND & NOR gates are called universal gates because by using them, we can implement any logic gate or any logic circuit e_{j} what is the 2's complement of (?34), 0? Ans: 234-binary number of [1110 1010], 1110 1010-15 converted to 1's-complement 1's complement of 234: 00010101 2's complement of 234's 1110/1001 The 7's complement of 234 is [11101010], 11s complement is obtained by replacing 1's by ols and o's by 11s. So i's complement ob 234 = .00010101. 21s complement is obtained by adding 1 to the its complement of the given number. So 24 complement of 234 = 00010101 000101


Represent the X-DR gate with minimum two NAND gates!

Ans: Step1: Draw ADIL And Dr Inventor) 10gic


+= AB+ AB

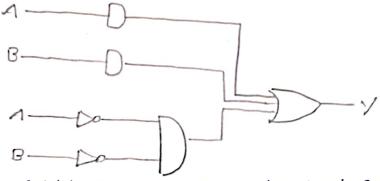

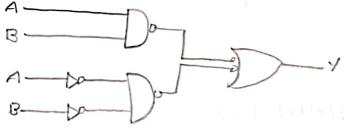
Step?:- Add bubbles at the output of ANDgate and input of OR-gate



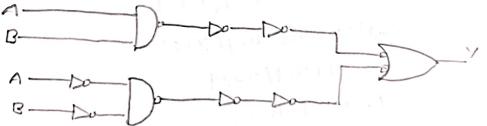
Step3: When bubbles one placed in that Particular Path, a place NOT gate




Stepy: - Eliminate double inversion.

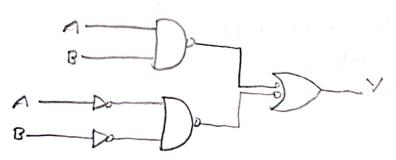

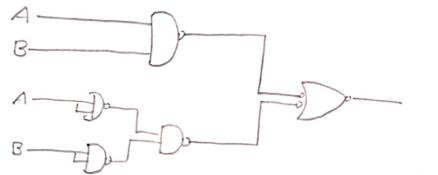Steps: Replace NOT-gate with Single input NAND-gate



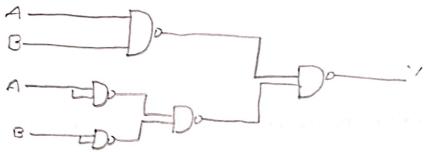Step6: - Replace input bubbled DR-gate with NAND gate.



b) Find the simplified boolean expression too the following function Y = (A+B)(A+C)(B+C)

Given Expression is

Ans.

$$Y = (A+B)(A+C)(B+C)$$

 $= (AA+AC+BA+BC)(B+C)$ (A. $A = AB$)
 $= (A+AC+BA+BC)(B+C)$
 $= (A(A+C+BA+BC)(B+C)$
 $= (A(A+C+BA+BC)(B+C)$
 $= (A(A+C+BC)(B+C)$
 $= (A+BC)(B+C)$
 $= ($

9 j Explain Duality theorem with example?

A:- Duality theosm says that, starting with boolean mendion, you can denive another booleen orelation by

I. changing each DR sign to AND sign

2. Changing each AND sign to DR sign

3. complementing any o cox) 1 appearing in the expression

ex: 1) Duar of A+ = 1

A. A = 0

State and Prove consensus theorm.

The consensus theorm is a Simplification dule in booleon argebra, which is particularly useful in digital logic design fox simplifying expressions.

The theorm states:


LHS: AB+A'C+BC

= AB+A'C+BC.1

d) what is the guay code equivalent of the (3A7) 16?

Ans: (3A7)16 - hexadecimal to binary

Gray code to binary (00110000111)

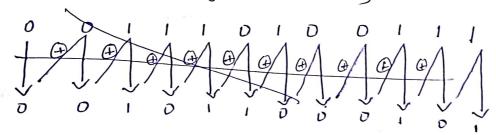

The binary code is (0010+1000+01),


e) Simplify (A9), in to decima!

Ans: Given Expression is (A9)16


= 169 *3*)

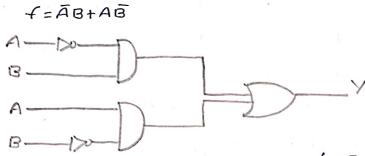a) Implement EX-DR gate using NOR-gates only


An: Step 1: - Draw ADI Logic tox given expression



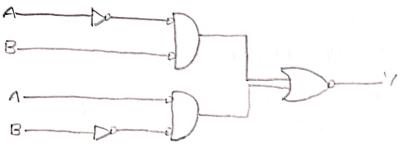
Step?:- Add bubbles at the output of OR gate and input of And Jate.



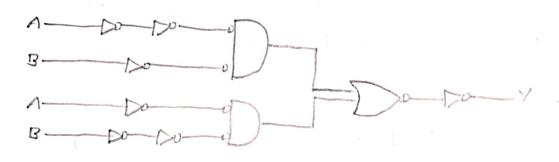
Step3: - when bubbies one placed in that path, place NOT gate




Step 4: Eliminate double invension

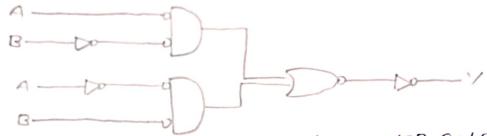

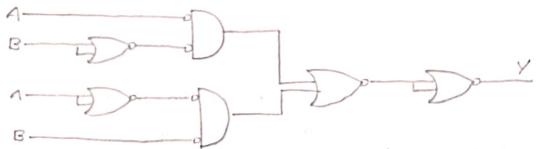Step 5: - Replace NOT gate with single input NOR gate



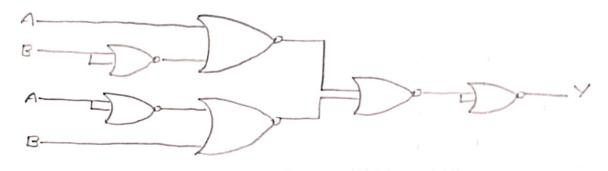Step6: Replace input bubbled AND gate with NOR gates



b) What is one's complement? Sho subtract 48 from 23 using one's complement subtraction method?

Ans: 1's complement: one's complement is a method of sepsesenting negation binary number in which all the bits of the number are inverted [i.e I's are changed to 0's and 0's are changed to 1's)

Subtract 48-23 using 1's complement.

The sesuit is +ve

1's complement of 25

To scuss the operation of basic rogic gates and universal gates using the table?

ans: ij AND Gate: An AND gate is a digital logic gate that outputs Iltane) only if all inputs one 1; Otherwise it outputs o (talse).

Touth Labie:

ii) OR-gate! - An OR-gate has two ox more input signals but a single output signal or gate produces output high when atteast one input is high, and when all inputs one low the output of or gate is low.

iii) NOT gate has one input and one output. The output is complement to the input


4) NAND gate: NAND gote may have one los) more inputs with only one output NAND gates produces the output as complement ilp i.e.it produces of high only when atleast one ilp is Low and produces of plow, when an inputs one high.


Touth tabie!

5) NOR-gate: NOR-gate may have one ox moxe ilp's with only one of NOR gate produces the Olp as complement of DR gate i.e it produce Olp high only when onlip's one now and the Olp is now if atteast on eilp is high.

4) Implement the following function using NAND gates F= AlB+co)+1Bc

Ans! Given Expression is F=A[B+CD]+[BC]

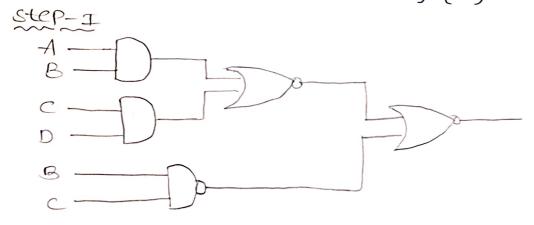

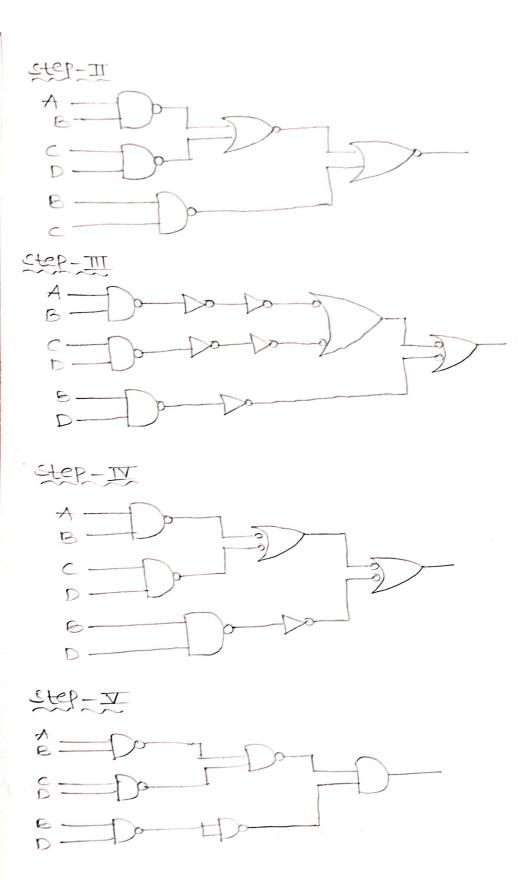

LHS:
$$A'BC+AB'C+ABC'+ABC'$$

$$= BC(A+A')+AB'C+ABC'$$

$$= BC+AB'C+ABC'$$

$$= BC+A[B'C+BC']$$

$$= BC+AB+AC$$

$$= AB+BC+AC.$$

i) what is the goay code of equavalent of the Heac Number 287


Pin hexis oolo in binary

Bin hexis low in binary

Fin hex is on in binary

50, 287 in hex is

0010 1011 0111 (binary)

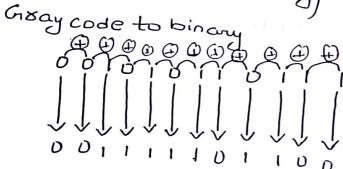

Thus the Group code equivarend is

= 001111101100