

| | | | | | | |
|---|---|-------------|------------|--------------------------|------------------------------|---------------------|
| St. Peter's Engineering College (Autonomous) Dullapally (P), Medchal, Hyderabad – 500100. I - Mid Term Examination – November 2023 | | | | Dept. | : | ECE/CSE/ CSD/CSC |
| | | | | Academic Year 2023-24 | | |
| Subject Code | : | AS22-02ES01 | Subject | : | Basic Electrical Engineering | |
| Class/Section | : | B. Tech. | Year | : | I | Semester : I |
| Duration | : | 120 Min | Max. Marks | : | 30 | Date: : |

| BLOOMS LEVEL | | | | | |
|--------------|----|------------|----|--------|----|
| Remember | L1 | Understand | L2 | Apply | L3 |
| Analyze | L4 | Evaluate | L5 | Create | L6 |

PART – A (10x1M = 10M)**Note: Answer all Questions. Each Question carries equal marks.**

| Q. No | Question (s) | Marks | BL | CO |
|-------------------|--|-------|----|--------|
| UNIT - I | | | | |
| 1 | a) State Ohms law? write down its limitations. | 1M | L1 | C114.1 |
| | b) Classify various network elements? | 1M | L1 | C114.1 |
| | c) State Maximum Power Transfer theorem | 1M | L2 | C114.1 |
| | d) Define current and voltage. | 1M | L2 | C114.1 |
| UNIT – II | | | | |
| | e) Define inductive reactance and write down the formula for it. | 1M | L1 | C114.2 |
| | f) Define power factor of an ac circuit. | 1M | L1 | C114.2 |
| | g) What is power triangle? | 1M | L1 | C114.2 |
| | h) Define resonant frequency? | 1M | L1 | C114.2 |
| UNIT – III | | | | |
| | i) Explain the working principle of a dc generator? | 1M | L2 | C114.3 |
| | j) What is the function of Commutator in a dc generator? | 1M | L2 | C114.3 |

PART – B (20M)

| Q. No | Question (s) | Marks | BL | CO |
|-----------------|---|-------|----|--------|
| UNIT - I | | | | |
| 2 | a) Obtain the volt-ampere relationship for R, L and C. | 4M | L2 | C114.1 |
| | b) Derive equivalent capacitance when two capacitances are connected in both series and parallel. | 4M | L3 | C114.1 |
| OR | | | | |

| | | | | |
|-------------------|--|-----------|-----------|---------------|
| 3 | State and explain Super position theorem by considering suitable example. | 8M | L2 | C114.1 |
| UNIT – II | | | | |
| 4 | a) Derive the Average value, Root mean square value, Form factor and Peak factor for half rectified Sine waveform. | 4M | L2 | C114.2 |
| | b) Derive the relationship among phase and line values for a Star connected network | 4M | L3 | C114.2 |
| OR | | | | |
| 5 | a) Derive the formula for impedance of series RLC circuit. | 4M | L2 | C114.2 |
| | b) A Series RLC circuit has $R=10\ \Omega$, $L=25\ \text{mH}$ and $C=60\ \mu\text{F}$ with frequency of 50 Hz. Determine the impedance and power factor of the circuit. | 4M | L3 | C114.2 |
| UNIT – III | | | | |
| 6 | Classify various DC Generators with neat diagrams and necessary equations | 4M | L2 | C114.3 |
| OR | | | | |
| 7 | Write down the applications of dc generators | 4M | L2 | C114.3 |
