

## IMPORTANT QUESTIONS

### Short answer questions:

- 1) Write short notes on binary number systems?
- 2) Why NAND and NOR gates are called Universal gates.
- 3) Convert Binary to Octal  $(011011011.011011100)_2$
- 4) Write about Idempotent Law and its Truth Table
- 5) Draw the block diagram of 4X1 MUX.
- 6) Write about min-term & max-term.
- 7) Realize following expression  $f = \sum_m (0,3)$  using K-Map.
- 8) Write the equation of POS =  $\prod_M (1,6,8,12)$
- 9) Write the Boolean expression for sum and carry of Half Adder
- 10) Write the Boolean expression for sum and carry of Full

### Subtractor.

- 11) Write Truth table and Circuit Diagram for XOR Gate and NOR Gate.
- 12) Convert Octal to binary number  $(562)_8$
- 13) Write about Distributive Law and write its Truth Table
- 14) Draw the logic circuit for the function  $F = A' + B C'$ .
- 15) Write about SOP & POS.
- 16) Define multiplexer.
- 17) Write the equation of SOP =  $\sum m(0,3,9,14,15)$
- 18) Draw the block diagram of 1X2 DEMUX.
- 19) Write the Boolean expression for sum and carry of Full Adder
- 20) Write the Boolean expression for sum and carry of Half

### Subtractor.

- 21) Convert Binary to Hexadecimal  $(11011011.01101110)_2$
- 22) State De-Morgan's Law.
- 23) Write about Absorption Law and write its Truth Table
- 24) Convert Hexadecimal to Decimal  $(A79.E4)_{16}$
- 25) Define K-map.

- 26) Define De-multiplexer.
- 27) Realize following expression  $f = \prod (0,1)$  using K-Map.
- 28) Write about min-term & max-term.
- 29) Write the Boolean expression for sum and carry of Full Adder
- 30) Write the Boolean expression for sum and carry of Full Subtractor

Long answer questions:

- 1) Implement XOR Gate using NOR.
- 2) Convert Binary code to Gray code the binary number is 01011101, and convert Gray code to Binary code the Gray code is 10110101
- 3) Do the 2's complement subtraction of  $26 - 41$  and Do 2's complement subtraction of  $010 - 01110$ .
- 4) Prove that  $AB + A'B + BC = AB + A'C$  and  $(A+C)(A'+B) = AB + A'C$ .
- 5) Simplify the equation using k-map  $f = \sum(0,2,3,4,6,7)$  draw the logic diagram also.
- 6) Write the truth table, Logic circuit and block diagram for 1x8 Demux.
- 7) Convert  $f = B + A'D + A'B'C + ABC + ABD'$  into standard SOP & standard POS
- 8) Implement the given function using 4x1 mux  $f(A,B,C) = \sum(1,3,5,6)$
- 9) Design 3-bit full adder
- 10) Design half adder and half subtractor.
- 11) Implement XNOR Gate using NAND
- 12) Prove that  $AB + A'B + BC = AB + A'C$  and  $(A+C)(A'+B) = AB + A'C$
- 13) Do the 1's complement subtraction of  $21 - 34$  and Do 1's complement of  $011 - 01000$ .
- 14) Convert Binary code to Gray code the binary number is 01011101, and convert Gray code to Binary code the Gray code is 10110101
- 15) Simplify the equation using k-map  $f = \sum(4,5,7,12,14,15) + d(3,8,10)$
- 16) Write the truth table, Logic circuit and block diagram for 1x8 Demux
- 17) Convert  $f = (A+C')(B+C)(A'+C)(B'+C)$  into standard POS & standard SOP
- 18) Do the 2's complement subtraction of  $26 - 41$  and Do 2's complement of  $010 - 01110$ .
- 19) Design 3-bit full subtractor
- 20) Design 3-bit full adder

- 21) Implement XNOR Gate using NAND
- 22) Do the 1's complement subtraction of  $21 - 34$  and Do 1's complement of  $011 - 01000$ .
- 23) Prove that  $AB + A'B + BC = AB + A'C$  and  $(A+C)(A'+B) = AB + A'C$
- 24) Do the 2's complement subtraction of  $26 - 41$  and Do 2's complement of  $010 - 01110$ .
- 25) Convert  $f = (A+C')(B+C)(A'+C)(B'+C)$  into standard POS & standard SOP
- 26) Simply the equation using k-map  $f = \sum(0,2,3,4,6,7)$  draw the logic diagram also
- 27) Implement the given using 8X1 MUX  $f(A,B,C,D) = \sum(1,3,4,5,6,11,15)$
- 28) Simply the equation using k-map  $f = \sum(4,5,7,12,14,15) + d(3,8,10)$
- 29) Design 3-bit full subtractor
- 30) Design half adder and half subtractor.