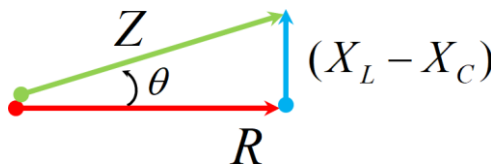
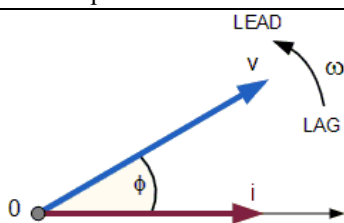
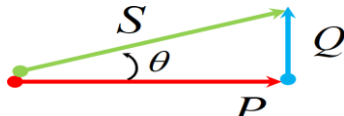
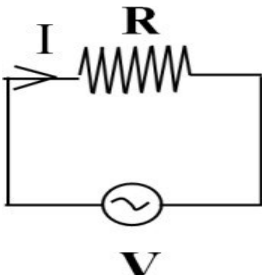
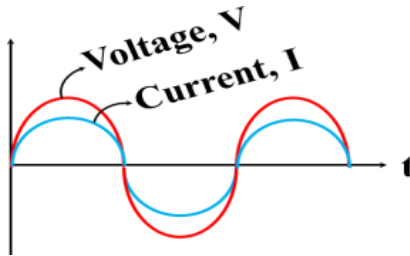

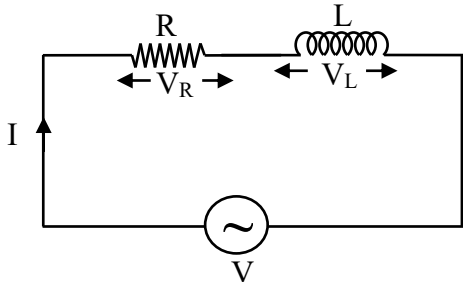


UNIT-II AC Circuits			
(1 Marks)			
1.	Taxonomy Level: Remember	CO: C114.2	PI: 3.2.3
	Define inductive reactance		
	Inductive reactance The opposition offered by an inductor in an AC circuit for the flow of current through it is called inductive reactance. It is represented by X_L and the units are ohms. $X_L = \omega L$		
2.	Taxonomy Level: Remember	CO: C114.2	PI: 3.2.3
	Define Impedance?		
	Impedance The opposition offered by an AC circuit for the flow of current through it is called impedance. It is represented by Z and the units are ohms. $Z = R + j(X_L - X_C)$		
3.	Taxonomy Level: Remember	CO: C114.2	PI: 3.2.3
	Define Power factor.		
	Power factor: It is the cosine of angle between voltage phasor to current phasor in AC circuits. Power factor, $p.f = \cos \theta$ $\cos \theta = \frac{R}{Z}$		
4.	Taxonomy Level: Remember	CO: C114.2	PI: 3.2.3
	Draw impedance triangle?		
	 <p>R = Resistance X_L = Inductive Reactance X_C = Capacitive Reactance Z = Impedance</p>		
5.	Taxonomy Level: Remember	CO: C114.2	PI: 3.2.3
	Define phase difference		
	It is the Difference between two phases or vectors.		
			
(3 Marks)			
1.	Taxonomy Level: Remember	CO: C114.2	PI: 3.2.3
	Define resonant frequency and derive the formula for it.		
	Resonant frequency The frequency at which inductive reactance is equals to capacitive reactance that frequency is called as resonant frequency.		


	$X_L = \omega L$ $X_C = \frac{1}{\omega C}$ <p>At Resonance</p> $X_L = X_C$ $\omega L = \frac{1}{\omega C}$ $\omega_r = \frac{1}{\sqrt{LC}}$ $f_r = \frac{1}{2\pi\sqrt{LC}}$		
2.	Taxonomy Level: Remember Mention the various types of powers in AC circuits& represent the power triangle.	CO: C114.2	PI: 3.2.3
	<p>There exist three powers in an AC circuit. Those are,</p> <ol style="list-style-type: none"> 1. Real Power 2. Reactive Power 3. Apparent Power <p>Power triangle for capacitive load is,</p> 		
3.	Taxonomy Level: Remember A series RLC network consists of $R=3\Omega$, $L=2\text{mH}$ and $C=0.4\mu F$. Determine the Angular resonant frequency.	CO: C114.2	PI: 3.2.3
	<p>Given data</p> $R=3\Omega$ $L=2\text{ mH}=2\times 10^{-3}\text{H}$ $C=0.4\mu F$ $\omega_r = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2\times 10^{-3} \times 0.4\times 10^{-6}}} = 35355.33\text{rad/sec}$		
4.	Taxonomy Level: Remember Find the impedance of R circuit with AC excitation	CO: C114.2	PI: 3.2.3
	<p>Circuit Diagram:</p>  <p>Voltage-Current-Impedance: $V = V_0 \sin \omega t$</p>		

	$I = \frac{V_0 \sin \omega t}{R}$ $I = I_0 \sin \omega t$ $Z = R$ <p>Phasor Diagram</p>  <p>Vector Diagram:</p> 			
5.	<table><tr><td>Taxonomy Level: Remember</td><td>CO: C114.2</td><td>PI: 3.2.3</td></tr></table> <p>What is the relationship among the phase and line values in a i) star and ii) delta connected networks?</p>	Taxonomy Level: Remember	CO: C114.2	PI: 3.2.3
Taxonomy Level: Remember	CO: C114.2	PI: 3.2.3		
	<p>i) Star connected Network:-</p> $V_{\text{Phase}} = \frac{V_L}{\sqrt{3}}$ $I_{\text{Phase}} = I_{\text{Line}}$ <p>ii) Delta Connected Network:-</p> $V_{\text{Phase}} = V_{\text{Line}}$ $I_{\text{Phase}} = \frac{I_L}{\sqrt{3}}$			
(5 Marks)				
1.	<table><tr><td>Taxonomy Level: Understand</td><td>CO: C114.2</td><td>PI: 3.2.3</td></tr></table> <p>Analyze series RL circuit and obtain the impedance triangle for the circuit if it is excited with ac supply</p>	Taxonomy Level: Understand	CO: C114.2	PI: 3.2.3
Taxonomy Level: Understand	CO: C114.2	PI: 3.2.3		
	<p>Consider a series RL circuit connected with alternating voltage $V = V_m \sin \omega t$ as shown in below diagram</p>  <p>In the above diagram the current passes through the RL circuit then it causes two voltage drops. Those are, Voltage Drop across pure resistance , $V_R = I \times R$ Voltage drop across pure inductance, $V_L = I \times X_L$</p>			

If we take voltage phasors then according to KVL, the addition of phasors is

$$\overline{V} = \overline{V_R} + \overline{V_L} = \overline{IR} + \overline{IX_L}$$

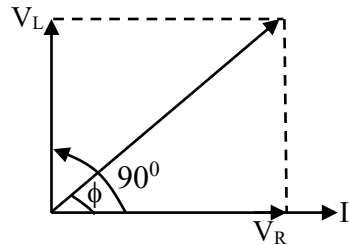From the above equation the phasor diagram and voltage triangle are obtained as,




Phasor diagram

From the above diagram

V_R is inphase with I

I lags V_L by 90°

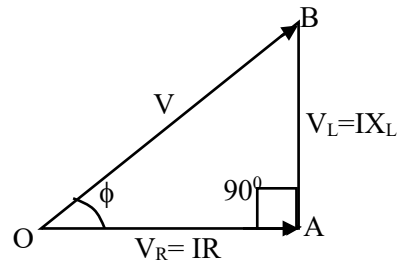

Voltage triangle

from $\angle OAB$

$$V = \sqrt{V_R^2 + V_L^2}$$


$$V = \sqrt{(IR)^2 + (IX_L)^2}$$

$$V = I \cdot \sqrt{R^2 + X_L^2}$$

$$V = I \cdot Z$$

Impedance & Impedance triangle :-

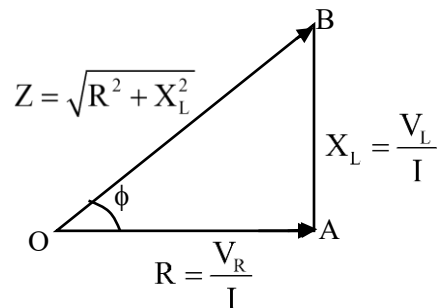The impedance for RL-series circuit is $Z = R + jX_L$ where $X_L = 2\pi fL$



From $\angle OAB$

$$\tan \phi = \frac{X_L}{R}$$

$$\sin \phi = \frac{R}{Z}$$

$$\cos \phi = \frac{X_L}{Z}$$

2. **Taxonomy Level: Understand** **CO: C114.2** **PI: 3.2.6**

A Series RLC circuit has $R=10\Omega$, $L=25\text{mH}$ and $C=60\mu F$ with frequency of 50Hz. Determine the impedance and power factor of the circuit.

Given data




$$R=10\Omega$$



$$L=25\text{ mH}=25\times 10^{-3}\text{H}$$


$$C=60\mu F$$

$$f=50\text{Hz}$$

	$\omega=2\pi f=2\times3.14\times50=314\text{rad/sec}$ $X_L=\omega L=314\times25\times10^{-3}=7.85\Omega$ $X_C=\frac{1}{\omega C}=\frac{1}{314\times60\times10^{-6}}=53.07\Omega$ $Z=\sqrt{R^2+(X_L-X_C)^2}$ $Z=\sqrt{10^2+(7.85-53.07)^2}$ $Z=53.43\Omega$ $\text{Power factor, } \cos \theta = \frac{R}{Z}$ $\cos \theta = \frac{10}{53.43}$ $\cos \theta = 0.99$			
3.	<table><tr><td>Taxonomy Level: Apply</td><td>CO: C114.2</td><td>PI: 3.2.6</td></tr></table> <p>A coil takes a current of 2 ampere at 0.6 lagging power factor from a 220 V, 50 Hz single phase source. If the coil is modeled by a series RL circuit, find the complex power in the coil and the values of R and L.</p>	Taxonomy Level: Apply	CO: C114.2	PI: 3.2.6
Taxonomy Level: Apply	CO: C114.2	PI: 3.2.6		
	<p>Given data</p> <p>$I=2\text{A}$</p> <p>$\cos\theta=0.6(\text{lag})$</p> <p>$V=220\text{V}$</p> <p>$f=50\text{Hz}$</p> <p>$S=?$</p> <p>$R=?$</p> <p>$L=?$</p> <p>Solution</p> $Z=\frac{V}{I}=\frac{220}{2}=110\Omega$ $R=Z\cos\theta=110\times0.6=66\Omega$ $\cos\theta=\frac{R}{Z}$ $X_L=\sqrt{(Z)^2-(R)^2}=88\Omega$ $X_L=\omega L$ $\omega=2\pi f=2\times3.14\times50=314\text{rad/sec}$ $L=\frac{X_L}{\omega}=\frac{88}{314}=0.28\text{H}$ $S=VI=220\times2=440\text{V}$			

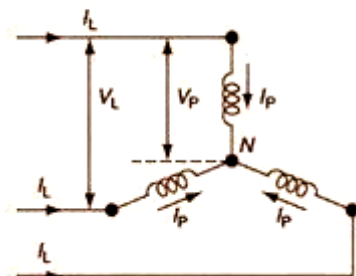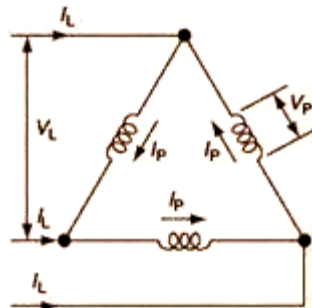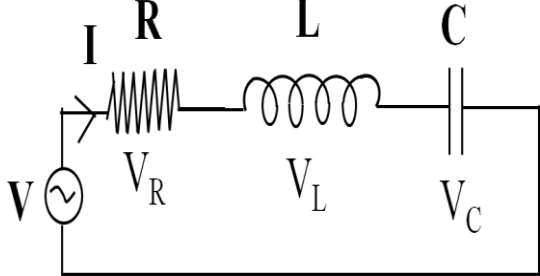4.	Taxonomy Level: Understand	CO: C114.2	PI: 3.2.3
Compare star and delta connections in three phase circuits			
	<p style="text-align: center;">Star Connection</p>  $V_{\text{Phase}} = \frac{V_{\text{Line}}}{\sqrt{3}}$ $I_{\text{Phase}} = I_{\text{Line}}$ <p>Power in single phase,</p> $P_{\text{ph}} = V_{\text{ph}} I_{\text{ph}} \cos \theta$ <p>Power in three phase,</p> $P = 3V_{\text{ph}} I_{\text{ph}} \cos \theta$ $P = \sqrt{3} V_L I_L \cos \theta$	<p style="text-align: center;">Delta Connection</p>  $V_{\text{Phase}} = V_{\text{Line}}$ $I_{\text{Phase}} = \frac{I_{\text{Line}}}{\sqrt{3}}$ <p>Power in single phase,</p> $P_{\text{ph}} = V_{\text{ph}} I_{\text{ph}} \cos \theta$ <p>Power in three phase,</p> $P = 3V_{\text{ph}} I_{\text{ph}} \cos \theta$ $P = \sqrt{3} V_L I_L \cos \theta$	
5.	Taxonomy Level: Understand	CO: C114.2	PI: 3.1.6
Derive the formula for impedance of series RLC circuit.			
	 $V_R = IR$ $V_L = IX_L$ $V_C = IX_C$ $V = V_0 \sin(\omega t + \theta)$ $V = \sqrt{V_R^2 + (V_L - V_C)^2}$ $V = \sqrt{(IR)^2 + (IX_L - IX_C)^2}$ $V = I\sqrt{(R)^2 + (X_L - X_C)^2}$ $Z = \frac{V}{I} = \sqrt{(R)^2 + (X_L - X_C)^2}$		

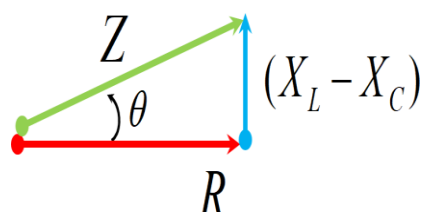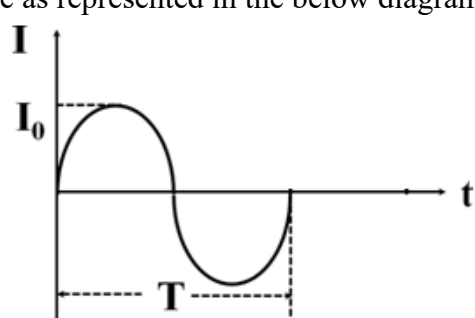	<p>Impedance Triangle:</p> 		
(10 Marks)			
1.	<p>Taxonomy Level: Understand</p> <p>Define Alternating quantity, Instantaneous value, Frequency, Time period and Cycle for a Full sine wave.</p>	CO: C114.2	PI: 4.1.1
	<p>Consider a full sine wave as represented in the below diagram,</p>  <p>Alternating quantity: The magnitude of the wave form varies with respect to time is called as alternating quantity.</p> <p>Instantaneous value: The value of an alternating quantity at a particular time is called as instantaneous value</p> <p>Frequency (f): Number of cycles per second is called as frequency it is represented by f and the units are Hz</p> $f = \frac{1}{T}$ <p>Time period (T): The time taken to complete one cycle is called time period it is represented by T and the units are seconds.</p> <p>Cycle: The positive and negative portions of a wave form is called Cycle.</p>		
2.	<p>Taxonomy Level: Understand</p> <p>Define the terms average value, rms value, form factor peak factor and derive them for full sine wave.</p>	CO: C114.2	PI: 4.1.1
	<p>Consider a full sine wave as represented below</p> <p>The wave form is represented in the equation form as,</p> $i(t) = I_m \sin \omega t$		

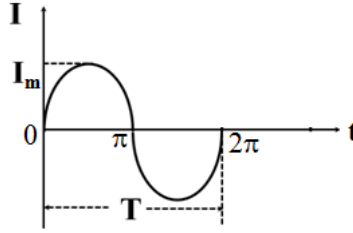

1. Average value:

The algebraic sum of all the instantaneous values over a period of time is called as average value. The average value can be obtained as,

$$I_{\text{avg}} = \frac{1}{\pi} \int_0^{\pi} i(t) dt$$

$$I_{\text{avg}} = \frac{1}{\pi} \int_0^{\pi} I_m \sin \omega t d\omega t$$

$$I_{\text{avg}} = \frac{I_m}{\pi} \int_0^{\pi} \sin \omega t d\omega t$$

$$I_{\text{avg}} = \frac{I_m}{\pi} [-\cos \omega t]_0^{\pi}$$

$$I_{\text{avg}} = \frac{2I_m}{\pi}$$

2. RMS value:

It is the DC equivalent of AC current. The rms value can be obtained as,

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$I_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (I_m \sin \omega t)^2 d\omega t}$$

$$I_{\text{rms}} = \sqrt{\frac{I_m^2}{2\pi} \int_0^{2\pi} \sin^2 \omega t d\omega t}$$

$$\text{We know, } \sin^2 \theta = \frac{1 - \cos 2\theta}{2}$$

$$I_{\text{rms}} = \sqrt{\frac{I_m^2}{2\pi} \int_0^{2\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) d\omega t}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2\pi}} \sqrt{\int_0^{2\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) d\omega t}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2\pi}} \sqrt{\left[\frac{1}{2} \int_0^{2\pi} d\omega t - \frac{1}{2} \int_0^{2\pi} \cos 2\omega t d\omega t \right]}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2\pi}} \sqrt{\left[\frac{1}{2} [\omega t]_0^{2\pi} - \frac{1}{2} [\sin 2\omega t]_0^{2\pi} \right]}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2\pi}} \sqrt{\pi - 0}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

	<p>3. from factor: The ratio of rms value to average value is called as form factor.</p> $\text{form factor} = \frac{\text{RMS value}}{\text{Average value}}$ <p>The form factor for the sine wave is,</p> $\text{form factor} = \frac{I_{\text{rms}}}{I_{\text{avg}}}$ $\text{form factor} = \frac{I_m / \sqrt{2}}{2I_m / \pi}, \text{ form factor} = 1.11$ <p>4. Peak factor: The ratio of peak value to rms value is called as peak factor.</p> $\text{peak factor} = \frac{\text{peak value}}{\text{rms value}}$ <p>The peak factor for the sine wave can be obtained as,</p> $\text{peak factor} = \frac{I_m}{I_m / \sqrt{2}}$ <p>Peak factor = 1.41</p>		
3.	<p>Taxonomy Level: Analyze</p> <p>Three similar coils each of resistance 40Ω and the inductance 2 H are connected in i) star and ii) delta to the three phase 50Hz and 440V supply. Calculate the line current and total Power absorbed.</p>	CO: C114.2	PI: 4.1.1
	<p>Given data $R = 40\Omega$, $L = 2\text{H}$ $F = 50\text{Hz}$, $\omega = 314 \text{ rad/sec}$ $X_L = \omega L = 314 \times 2 = 628\Omega$ $Z_{\text{ph}} = \sqrt{(R)_L + (X_L)} = 629.27 \Omega$</p> <p>i) Star connected</p> $V_{\text{Phase}} = \frac{V_{\text{Line}}}{\sqrt{3}} = \frac{440}{\sqrt{3}} = 254.03\text{V}$ $I_{\text{phase}} = \frac{V_{\text{phase}}}{Z_{\text{phase}}} = \frac{440}{629.27} = 0.699\text{A}$ $I_{\text{Line}} = I_{\text{Phase}} = 0.403 \text{ A}$ $P = 3 \times 440 \times 0.699 \times 0.063 = 58.12\text{W}$ $\cos \theta = \frac{R}{Z} = \frac{40}{629.27} = 0.063$ $P = 3 \times 254.03 \times 0.403 \times 0.063 = 19.34\text{W}$ <p>ii) Delta connected</p> $V_{\text{Phase}} = V_{\text{Line}} = 440\text{V}$ $I_{\text{Phase}} = \frac{V_{\text{Phase}}}{Z_{\text{Phase}}} = \frac{254.03}{629.27} = 0.403 \text{ A}$ $P = 3V_{\text{ph}} I_{\text{ph}} \cos \theta = 3 \times 440 \times 0.403 \times 0.063 = 33.5\text{W}$		